

**Exam - Computer Architecture Unit I [08/02/2023] (A)**

Surname: \_\_\_\_\_ Name: \_\_\_\_\_

Student ID Number (Matricola): \_\_\_\_\_

**DSA Students should solve only the first 4 exercises (grade will be scaled accordingly)**


**Exercise 1 (8 points)**

Design a sequential circuit with two inputs  $x_1, x_0$  that encode the characters A, L, F as follows:

$x_1, x_0$	character
00	A
01	L
1-	F

The circuit has 2 outputs  $z_1$  and  $z_0$ . The state machine outputs  $z_1=1$  when it receives on the input the sequence ALA, and outputs  $z_0=1$  when it receives on the input the sequence ALFA. Overlaps are allowed. Draw the circuit.

**Solution:**

 

**State encoding:**

<b>R</b>	<b>00</b>
<b>A</b>	<b>01</b>
<b>AL</b>	<b>10</b>
<b>ALF</b>	<b>11</b>

**Next state and output table:**

CS	$S_1$	$S_0$	$x_1$	$x_0$	NS	$S_1'$	$S_0'$	$z_1$	$z_0$
R	0	0	0	0	A	0	1	0	0
R	0	0	0	1	R	0	0	0	0
R	0	0	1	-	R	0	0	0	0
A	0	1	0	0	A	0	1	0	0
A	0	1	0	1	AL	1	0	0	0

A	0	1	1	-	R	0	0	0	0
AL	1	0	0	0	A	0	1	1	0
AL	1	0	0	1	R	0	0	0	0
AL	1	0	1	-	ALF	1	1	0	0
ALF	1	1	0	0	A	0	1	0	1
ALF	1	1	0	1	R	0	0	0	0
ALF	1	1	1	-	R	0	0	0	0

Derive next state and output equations, and then draw the circuit (with gates, ROM, PLA, or whatever you prefer)

**Exercise 2 (6 points)** A combinational circuit has a 4 bit input  $A=a_3a_2a_1a_0$  representing a two's complement number, and outputs  $Z=z_1z_0$  as an unsigned binary number, such that:

$Z=0$  if  $3 \leq A \leq 7$

$Z=1$  if  $-3 \leq A < 3$

$Z=2$  if  $-7 \leq A < -3$

$Z=3$  if  $A=-8$

Write down:

- The corresponding truth table
- The minimal POS form for  $z_1$
- The all-NAND and all-NOR form for  $z_1$  (NOT gates are allowed, i.e., you don't need to translate NOT with NAND/NOR)
- $z_1$  using only three 2:1 multiplexers

**Solution:**

**Truth Table:**

$a_3$	$a_2$	$a_1$	$a_0$	$z_1$	$z_0$
0	0	0	0	0	1
0	0	0	1	0	1
0	0	1	0	0	1
0	0	1	1	0	0
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	0	0
1	0	0	0	1	1
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	1	0
1	1	0	0	1	0
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	0	1

**Minimal POS form for  $z_1$ :**

		a3 a2			
		00	01	11	10
a1 a0	00	0	0	1	1
	01	0	0	0	1
	11	0	0	0	1
	10	0	0	0	1

$$z_1 = (\sim a_2 + \sim a_0) * (\sim a_2 + \sim a_1) * (a_3)$$


**all-NAND form for  $z_1$ :**

$$z_1 = \sim(\sim(\sim(a_2 * a_0) * \sim(a_2 * a_1)) * (a_3))$$

**all-NOR form for  $z_1$ :**


$$z_1 = \sim(\sim(\sim a_2 + \sim a_0) + \sim(\sim a_2 + \sim a_1) + (\sim a_3))$$

**$z_1$  using MUX:**

 

**Exercise 3 (5 points)**

Analyze the state machine shown in the figure. Write down next state and output tables and draw the state transition diagram.

 **Solution:**


It is a Moore FSM (output does not depend on the input).

**Outputs table + state encoding**

$y_0$	$y_1$	$z$	Stato
0	0	0	S0
0	1	1	S1
1	0	0	S2
1	1	0	S3

**Next state table**

$y_0$	$y_1$	CS	$x$	$y_0'$	$y_1'$	NS
0	0	S0	0	0	0	S0
0	0	S0	1	1	1	S3
0	1	S1	0	1	0	S2
0	1	S1	1	1	1	S3
1	0	S2	0	0	1	S1
1	0	S2	1	1	0	S2
1	1	S3	0	1	1	S3
1	1	S3	1	1	0	S2

 

#### Exercise 4 (3 points)


Draw the state transition diagram described by the following SystemVerilog code:

```

module fsm2(input logic clk, reset,
            input logic a, b,
            output logic y);
  logic [1:0] state, nextstate;
  parameter S0 = 2'b00;
  parameter S1 = 2'b01;
  parameter S2 = 2'b10;
  parameter S3 = 2'b11;
  always_ff @(posedge clk, posedge reset)
    if (reset) state <= S0;
    else state <= nextstate;
  always_comb
    case` (state)
      S0: if (a ^ b) nextstate = S1;
          else nextstate = S0;
      S1: if (a & b) nextstate = S2;
          else nextstate = S0;
      S2: if (a | b) nextstate = S3;
          else nextstate = S0;
      S3: if (a | b) nextstate = S3;
          else nextstate = S0;
    endcase
  assign y = (state == S1) | (state == S2);
endmodule

```

**Solution:**

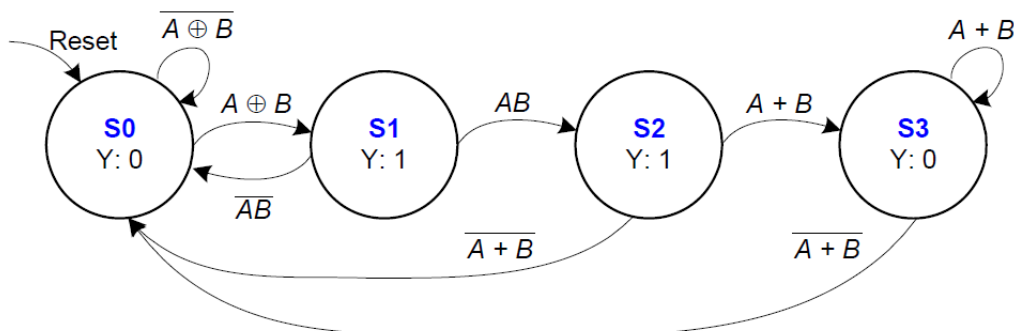

### Exercise 5 (4 points)

Given  $X = -1614$  and  $Y = 675$  represented in base 10:

- Convert them to two's complement numbers using the minimum number of bits necessary to represent both values
- Compute  $X+Y$  and  $X-Y$
- Convert the results to base 10 number and check their correctness
- Convert  $X$  and  $Y$  to IEEE 754 half-precision representation

#### Solution:

##### Base 2 conversion:

$$1614 = 011001001110 \Rightarrow -1614 = 100110110010$$

$$675 = 001010100011$$

##### Sum, subtraction, and base 10 conversion:

$$\begin{array}{r} X+Y = 100110110010 + \\ \quad 001010100011 = \\ \hline \end{array}$$

$$110001010101 = -939 = -1614+675$$

$$-675 = 110101011101$$

$$\begin{array}{r} X-Y = 100110110010 + \\ \quad 110101011101 = \\ \hline \end{array}$$

$$011100001111 = \text{Overflow! } -1614 - 675 = -2289 \text{ (11 bit are not enough, they can only represent up to } -2048)$$

##### Half-precision conversion

$$1614 = 011001001110.0 = 1.1001001110 \cdot 2^{10}$$

$$X = -1614:$$

$$\text{Sign} = 1$$

$$\text{Exponent} = 10_{10}$$

$$\text{Exponent} + \text{bias} = 10_{10} + 15_{10} = 25_{10} = 11001_2$$

$$\text{Fraction} = 1001001110_2$$

$$\text{IEEE: } 1 \ 11001 \ 1001001110$$

$$Y = 675 = 001010100011 = 1.010100011 \cdot 2^9$$

$$\text{Sign} = 0$$

$$\text{Exponent} = 9$$

$$\text{Exponent} + \text{bias} = 9 + 15 = 24 = 11000$$

$$\text{Fraction} = 010100011$$

$$\text{IEEE} = 0 \ 11000 \ 0101000110$$

### Exercise 6 (4 points)

Given the expression  $f = (\overline{a(a + \overline{bcd})} + \overline{e}) \oplus (e + cd)$  simplify it and bring to minimal POS form.

#### Solution:

$$f = (\overline{a(a + \overline{bcd})} + \overline{e}) \oplus (e + cd)$$

$$= (\overline{a + abcd} + \bar{e}) \oplus (e + cd)$$

$$= (\bar{a} + \bar{e}) \oplus (e + cd)$$

$$= \overline{(\bar{a} + \bar{e})(e + cd)} + (\bar{a} + \bar{e})\overline{(e + cd)} =$$

$$= ae(e + cd) + (\bar{a} + \bar{e})\bar{e} \cdot \overline{cd} = ae + \bar{e} \cdot (\bar{c} + \bar{d}) = ae + \bar{c}\bar{e} + \bar{d}\bar{e} =$$

$$(a + \bar{c} + \bar{d})(a + \bar{c} + \bar{e})(a + \bar{d} + \bar{e})(a + \bar{e})(e + \bar{c} + \bar{d}) = (a + \bar{e})(a + \bar{c} + \bar{d})(\bar{c} + \bar{d} + e) =$$

$$(a + \bar{e})(\bar{c} + \bar{d} + e)$$